Digital Logic (BIT 103) Practical Report Manual:

1) Report should be written in A4 size paper

2) Question / Title:

3) Objectives:

4) Requirements:

i) Digital Logic Kit and Simulator
ii) 5 v Battery
iii) Logic gates/Logic Circuit
iv) Connecting wires
v) Interactive/ Sequence generator as input
vi) LED as Output

5) Theory

i) Introduction
ii) Functional Expression/Logic Expression
iii) Circuit Diagram
iv) Truth Table

6) Conclusion

Practical.1. Realize three input AND, OR, NAND and NOR gates with logic diagram and truth table.

i) AND Gate:

Practical.2 Realize the given Boolean functions with logic diagram and truth table

i) F1 = X' Y Z + X Y' Z + X' Y' Z' +X Z'
ii) F2 = (W' + X' + Y)'. Z